



جامعة الأهرام الكندية  
AHRAM CANADIAN UNIVERSITY

# Lecture (01)

## Ohm's and Kirchhoff's laws


---

Dr. Ahmed M. ElShafee

# Ideal basic circuit element

---

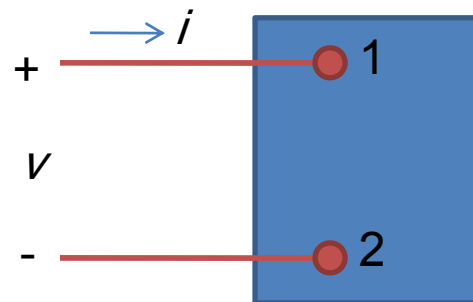
1. Has only 2 terminal
2. Described mathematically in terms of voltage and current
3. It can't be divided.


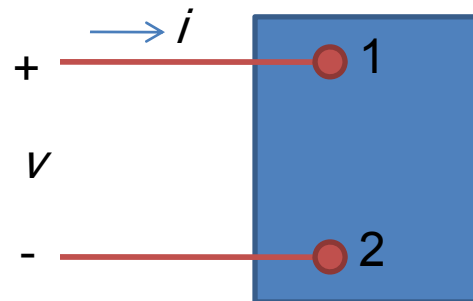
# Passive sign convention theory

---

- Passive sign convention:  
if the current reference direction is in the direction of the voltage drop across the element, +ve sign in any expression relates voltage to the current, otherwise use a -ve sign.
- Note: polarity reference is independent on function of the basic element, or its interconnection.



# Power and Energy

---

- Power and energy calculations are so important in electric circuit analysis because
  1. The useful output of these systems often nonelectrical (heat, light, movement, ....).
  2. All practical devices have limitations on the amount of power that can handle.

# Power and Energy (2)

---

- Passive sign convention

if the current flow is in the same direction of voltage drop,  
then

$$P = i \times v$$


*dissipating, absorbing power*

if not


$$P = -i \times v$$

*generating, losing power*


# Power and Energy (3)

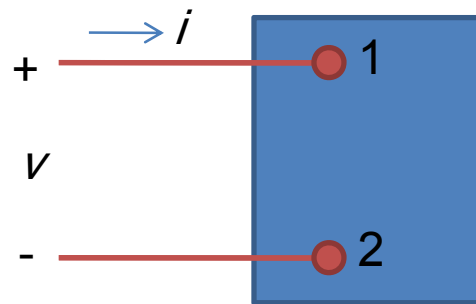


$$P = vi$$

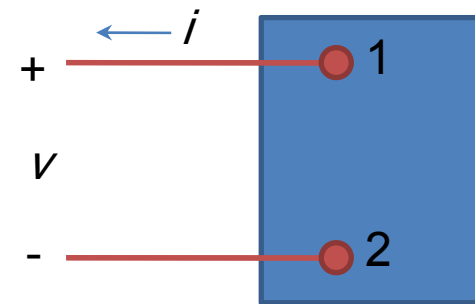

$$P = -vi$$

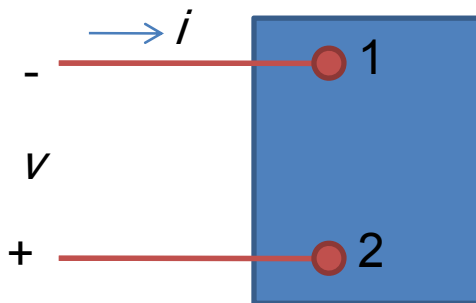

$$P = -vi$$

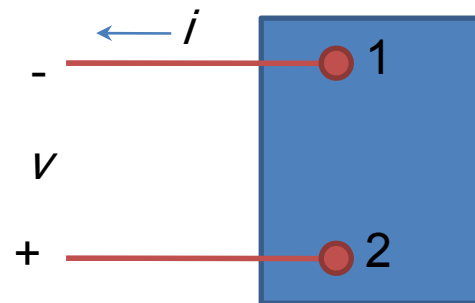


$$P = vi$$

# Power and Energy (4)

---

- Example: in the following model

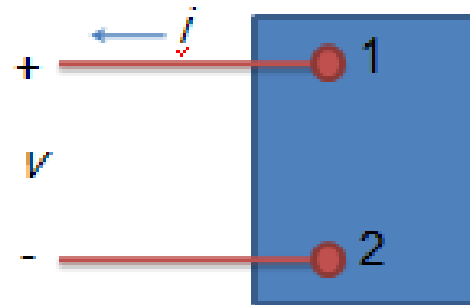

if  $i = 4$  A and  $v = -10$ V


then  $P = - (-10)(4) = 40$  W

The element is absorbing (dissipating) 40 watts

# Power and Energy (5)

---

- Example: in the following model

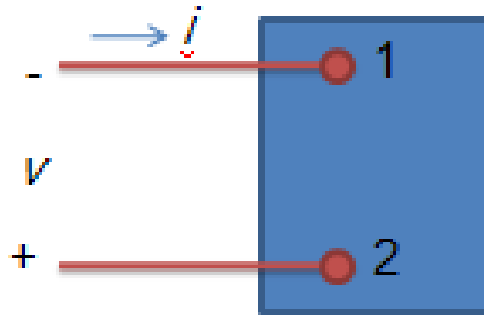

if  $i = -4$  A and  $v = 10$  V

then  $P = - (10)(-4) = 40$  W

The element is absorbing (dissipating) 40 watts




# Example 01

---

Assume that a 10V drop occurs across an element from terminal 2 to terminal 1 and that a current of 4A enters terminal 2.

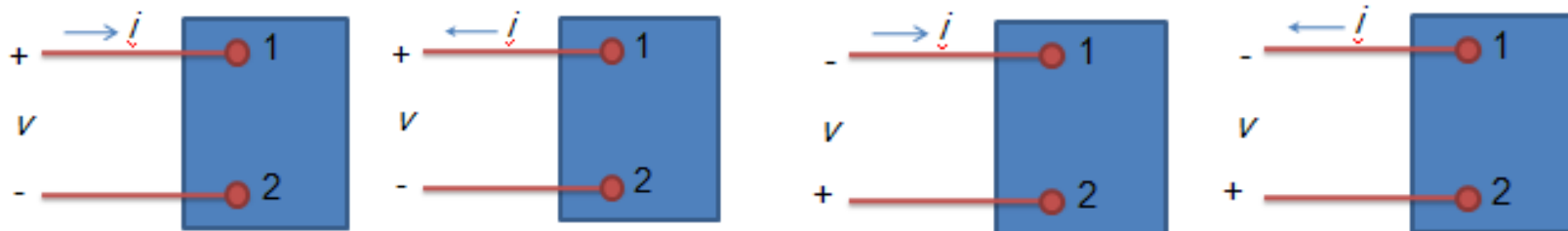- a) Specify the values of  $v$  and  $i$  for the polarity references shown in figures.
- b) State whether the circuit inside the box is absorbing or delivering power.
- c) How much power is the circuit absorbing?



# Answer 01

- Start with sketching the circuit model

- For the first model




$$v = -20\text{V} \quad i = -4\text{A};$$

$$P = (-20) \times (-4) = 80\text{W}, \text{ absorbing}$$

- For the second model

$$v = -20\text{V} \quad i = 4\text{A};$$

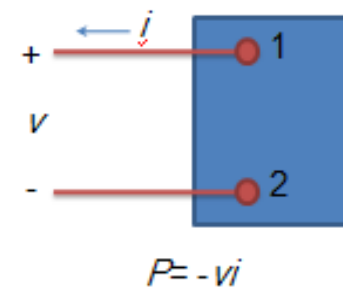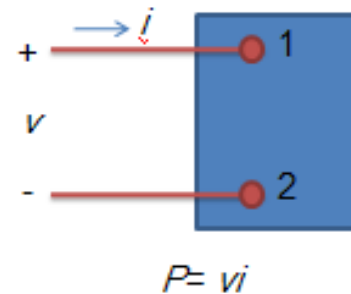
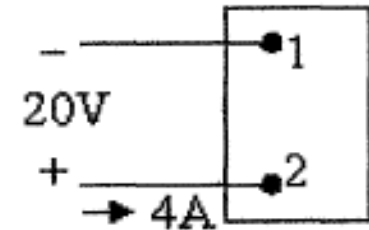
$$P = -(-20) \times (4) = 80\text{W}, \text{ absorbing}$$


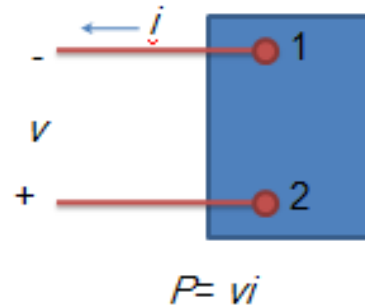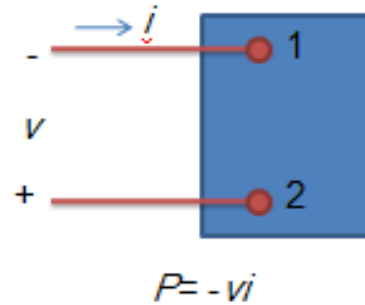
# Answer 01(2)

---

- For the 3<sup>rd</sup> model  
 $v = 20\text{V}$        $i = -4\text{A}$ ;  
 $P = -(20) \times (4) = 80\text{W}$ , absorbing
- For the 4<sup>th</sup> model  
 $v = 20\text{V}$        $i = 4\text{A}$ ;  
 $P = (20) \times (4) = 80\text{W}$ , absorbing




# Ohm's law

---

The voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor.
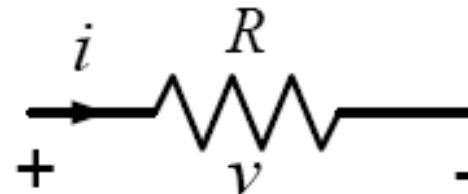
$$1 \text{ Ohm} : \begin{aligned} v &\propto i \\ v &= iR \end{aligned}$$





# Ohm's law (2)

---

Passive sign convention:

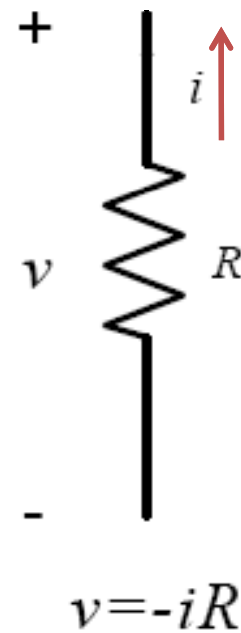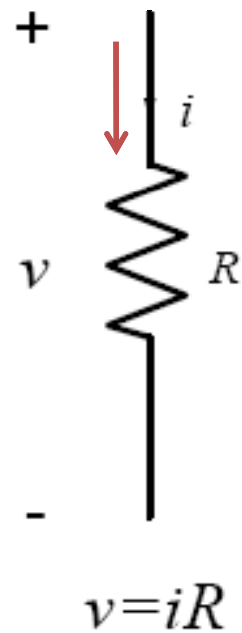There are two possible reference choices for the current and voltage



# Ohm's law (3)

---

Conductance is the opposite of resistance:

$$G = 1/R = i/v$$

Symbol: G

Units: Siemens (S) or mho ( $\overline{\Omega}$ )


# Ohm's law (4)

---

Power dissipated by a resistor:

$$p = vi = v\left(\frac{v}{R}\right) = \frac{v^2}{R}$$





$$p = vi = (iR)i = i^2 R$$

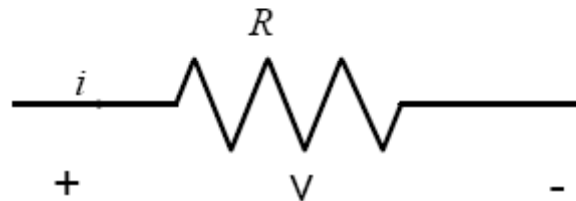

# Example 09

For each figure, calculate;

1.  $V_g$  and  $I$ .
2. Power.

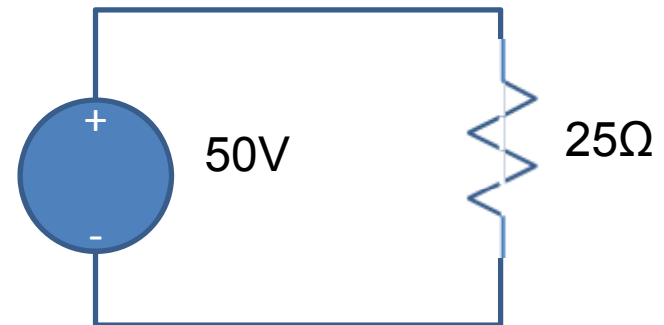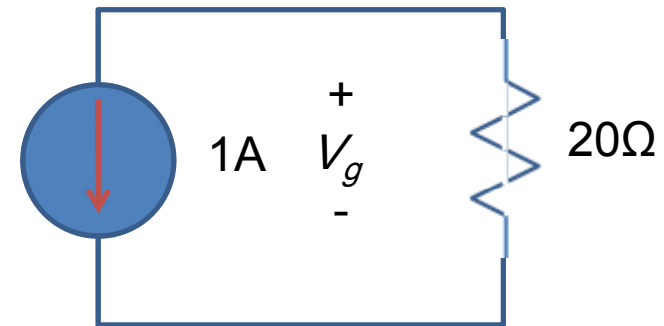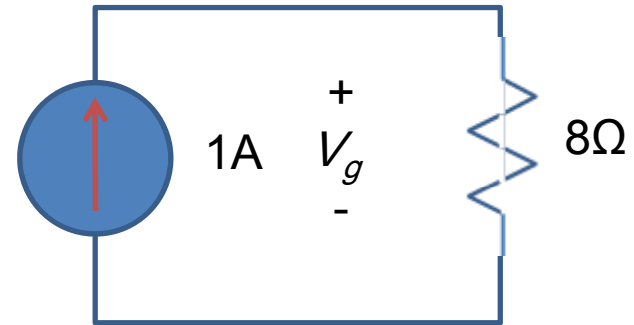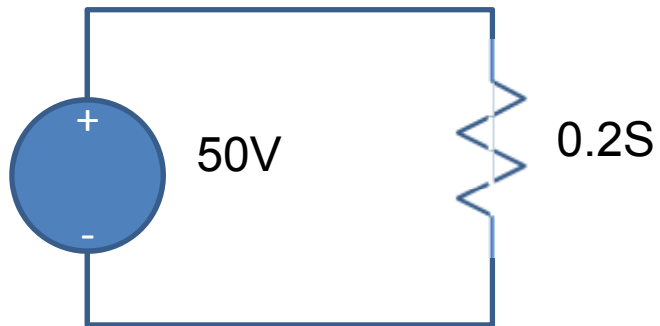



# Answer 09

---

$$I = 1A$$



$$V = I \cdot R = 8V$$

$$P = V^2/R = 8W$$

$$I = 1A$$

$$V = -I \cdot R = -20V$$

$$P = V^2/R = 20W$$

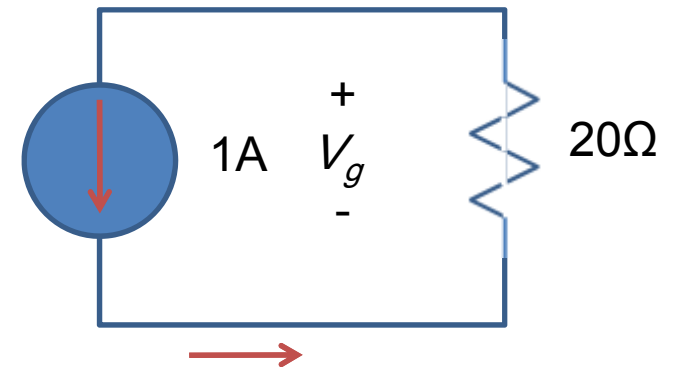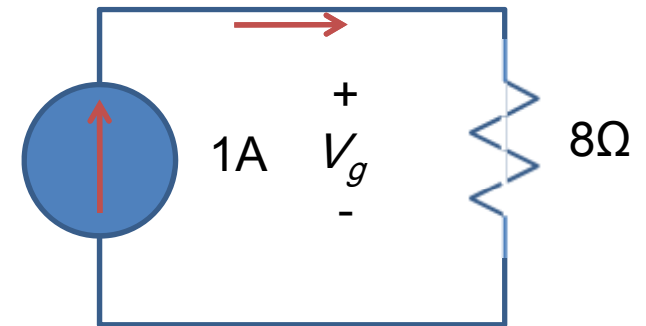


# Answer 09 (2)

---

$$V = 50V$$

$$I = V \cdot G = 10A$$


$$P = I^2 / G = 8W$$

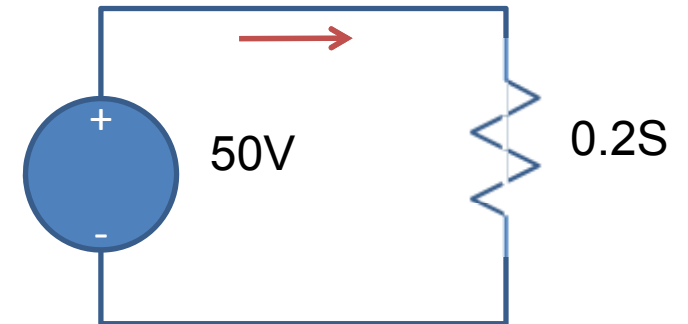

$$V = 50V$$

$$I = V / R = 2A$$


$$P = I^2 \cdot R = 100W$$

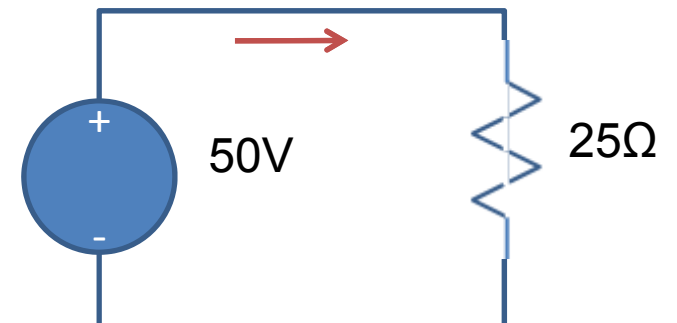

# Example 10

---

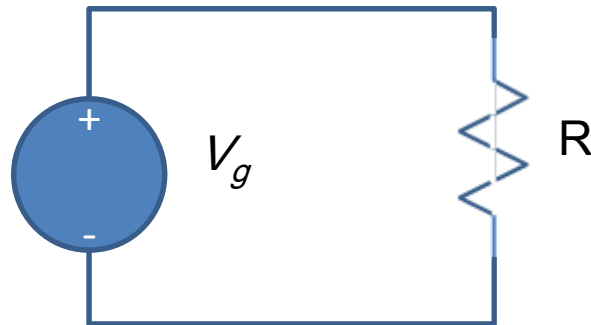- a.  $V_g = 1\text{KV}$ ,  $I_g = 5\text{mA}$ , find  $R$  &  $P_{\text{resistor}}$
- b.  $I_g = 75\text{mA}$ ,  $P_{\text{source}} = -3\text{W}$ , find  $V_g$ ,  $R$ ,  $P_{\text{resistor}}$
- c.  $R = 300\Omega$ ,  $P_{\text{resistor}} = 480\text{mW}$ , find  $I_g$ ,  $V_g$ .




# Answer 10

---

a)  $V_g = 1\text{KV}$ ,  $I_g = 5\text{mA}$ . find  $R$  &  $P_{\text{resistor}}$

$$R = V_g / I_g = 10^3 / 5 \times 10^{-3} = 0.2 \times 10^6 = 200\text{K}\Omega.$$

$$P = V \cdot I = 5\text{W}.$$

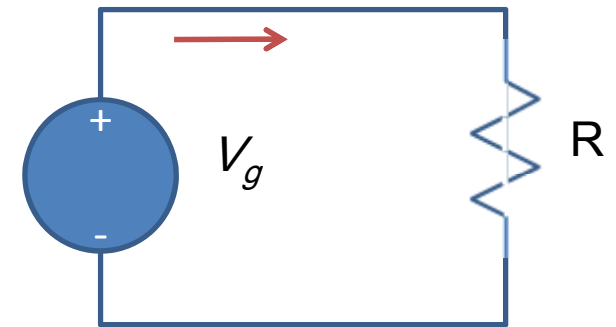

b)  $I_g = 75\text{mA}$ ,  $P_{\text{source}} = -3\text{W}$ . find  $V_g$ ,  $R$ ,  $P_{\text{resistor}}$

$$V_g = -P / I_g = -(-3 / (75 \times 10^{-3})) = 40\text{V}.$$

$$R = V_g / I_g = 40 / (75 \times 10^{-3}) = 533.33\Omega.$$

$$P_{\text{resistor}} = 3\text{W}.$$


## Answer 10 (2)

---

$R=300\Omega$ ,  $P_{\text{resistor}}=480\text{mW}$ , find  $I_g$ ,  $V_g$ .

$$I_g = (P/R)^{0.5} = ((480 \times 10^{-3})/300)^{0.5} = 0.04\text{A} = 40\text{mA}.$$

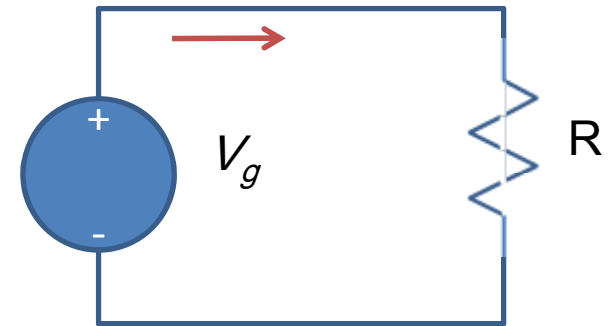
$$V_g = (P \times R)^{0.5} = ((480 \times 10^{-3}) \times 300)^{0.5} = 12\text{V}.$$


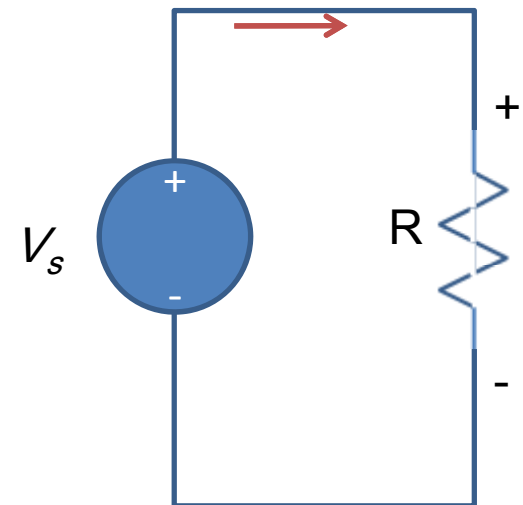
# Kirchhoff's laws


---

- Simple circuit
  - Voltage
  - Current
  - Power


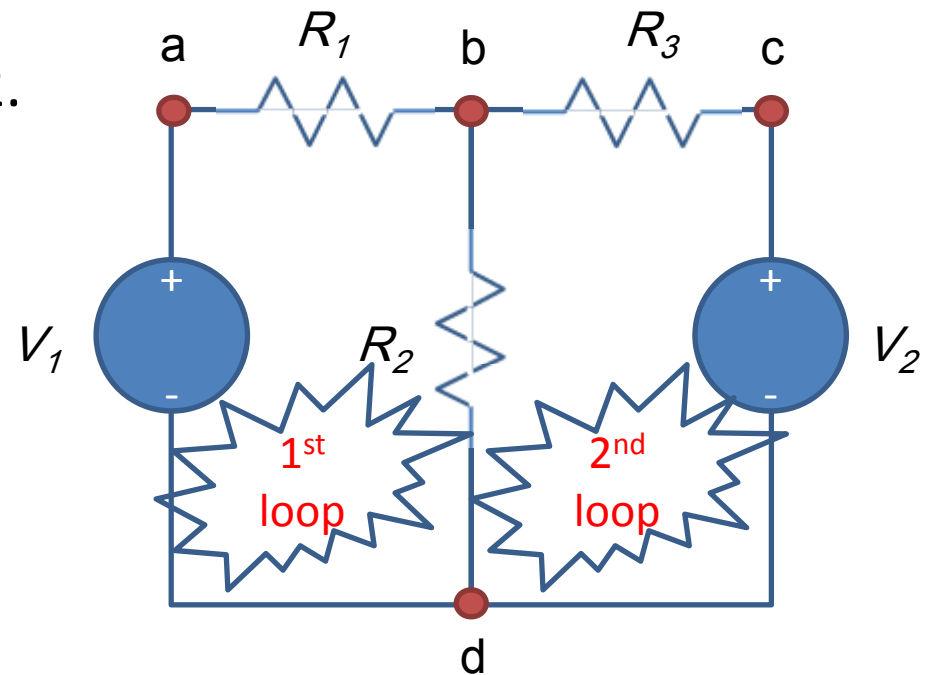
# Kirchhoff's laws (2)

- More Complex circuit,
  - Circuit contains 2 loops 1, 2.
  - bd branch shared between the two loops.
  - Nodes b, d are shared between the two loops.



# Kirchhoff's laws (3)

---

## Kirchhoff's Voltage Law (KVL):

“The algebraic sum of all voltage drops around any closed loop is zero”

$$\sum_{m=1}^M v_m = 0$$

$M$ : number of voltages in the loop


$V_m$ :  $m^{\text{th}}$  element voltage.

- Satisfied around all loops of a circuit.
- The law is about energy conservation


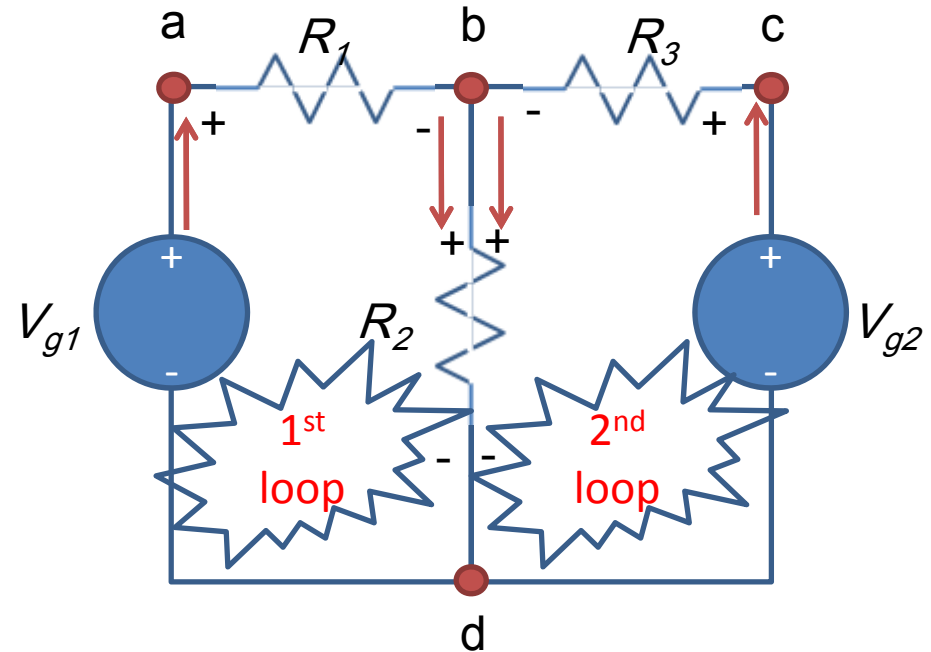
# Kirchhoff's laws (4)

- KVL example:
- 1<sup>st</sup> loop:  
$$-V_{g1} + V_1 + V_2 = 0$$
- 2<sup>nd</sup> loop:  
$$-V_{g2} + V_3 + V_2 = 0$$



- Passive sign convention:

Voltage get +ve if the current flow in side component is in the same direction of voltage drop, otherwise voltage get -ve sign.

# Kirchhoff's laws (5)

---

- **Kirchhoff's current Law (KCL):**

“The algebraic sum of currents around a node is zero”

$$\sum_{n=1}^N i_n = 0$$

$N$ : number of branches connected to the node

$i_n$ : h current entering the node

- Satisfied at all nodes of a circuit
- The law is about charge conservation

# Kirchhoff's laws (6)

- KCL example:


node a:  $-I_{g1} + I_1 = 0$

Node b:  $-I_1 - I_3 + I_2 = 0$

Node c:  $-I_{g2} + I_3 = 0$

Node d:  $-I_2 + I_{g1} + I_{g2} = 0$

So:  $I_2 = I_{g1} + I_{g2}$ .

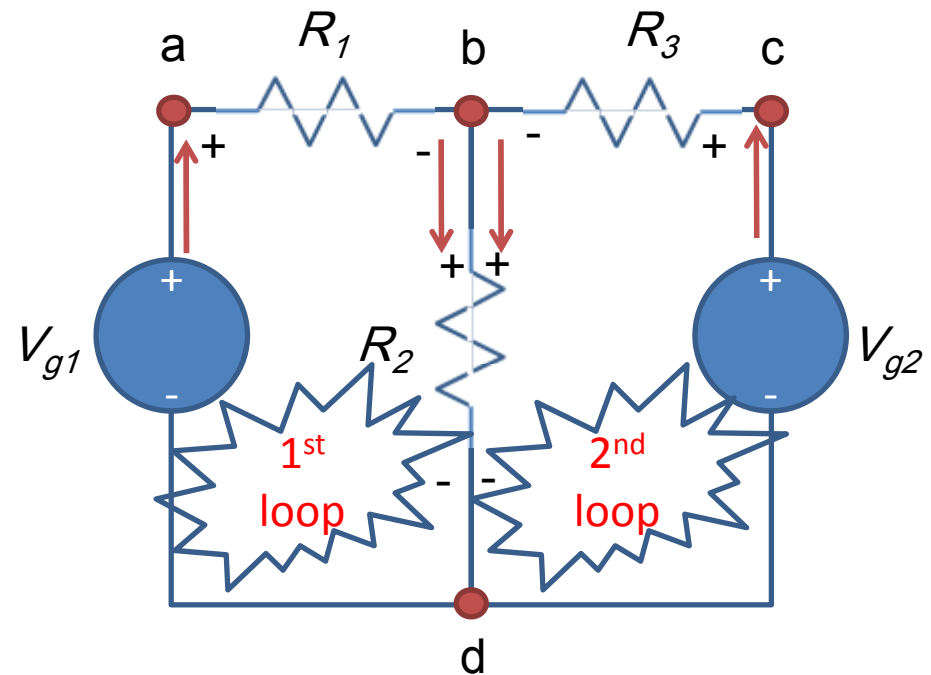

- Passive sign convention:


Current gets +ve if the current leave the node is while gets -ve sign if the current entering the node.

# Example 3

---

use KL and Ohm's law to

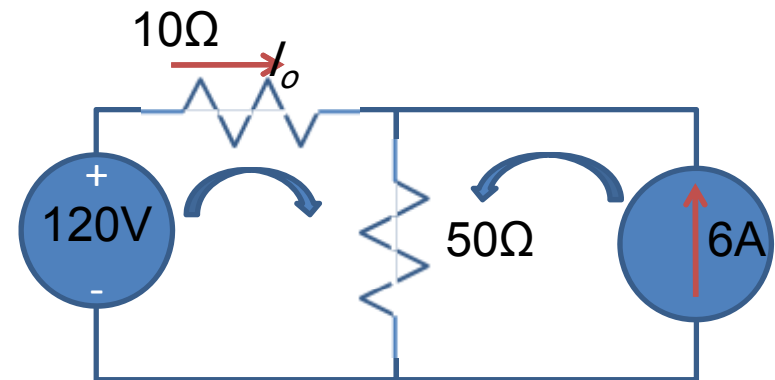1. find  $I_o$
2. *Verify that total dissipated power – total generated power*



# Example 3 solution

---

KCL:

$$-i_o - 6 + i_{50} = 0$$

$$i_{50} = i_o + 6 \dots\dots\dots(1)$$


KVL:

$$-120 + (10 \times i_o) + (50 \times i_{50}) = 0$$
$$\dots\dots\dots(2)$$

Submit 2 in 1

$$(10 \times i_o) + (50 \times (i_o + 6)) = 120$$

$$i_o = -3A$$

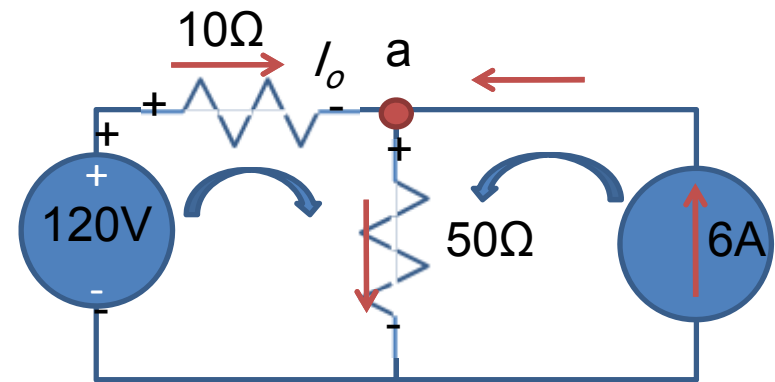

## Example 3 solution (2)

---

$$I_{50} = 3A$$

$$P_{10} = (i_o)^2 \times 10 = 9 \times 10 = 90W$$


$$P_{50} = 9 \times 50 = 450W$$

$$P_{120V} = -120 \times -i_{120V} = 360W$$

$$\text{Total dissipated power} = 360 + 90 + 450 = 900W$$

$$V_{50} = 50 \times 3 = 150V$$
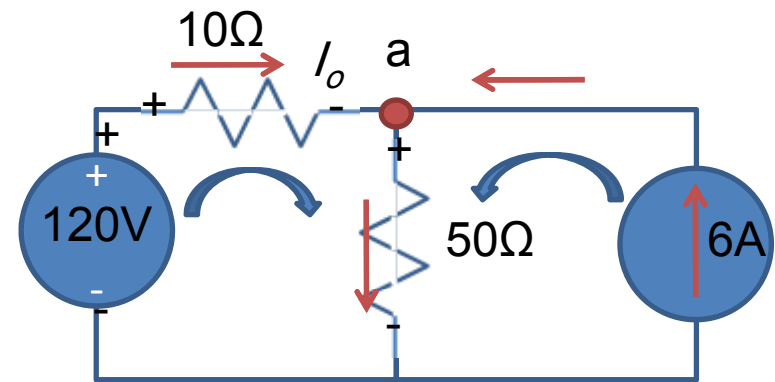
$$P_{6A} = -V_{50} \times 6 = -150 \times 6 = -900W \text{ (generated)}$$



# Example 4

---

For the shown circuit;

Find


$$I_s.$$

$$V_3.$$

$$V_2.$$

$$V_7$$

Power delivered by source.

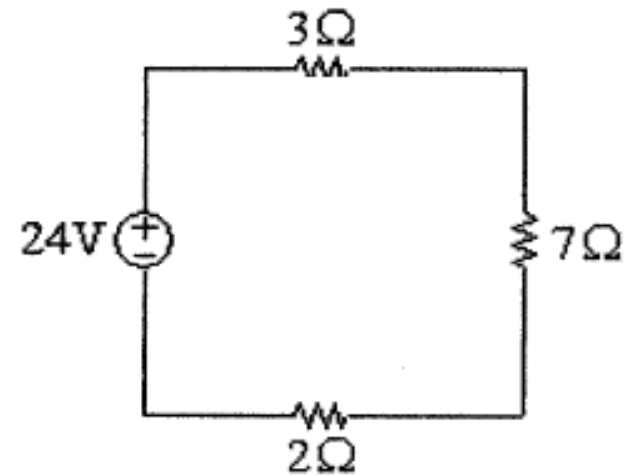

# Example 4 solution

---

KVL:

$$-24 + 3i_s + 7i_s + 2i_s = 0$$

$$12i_s = 24$$

$$i_s = 2A \quad \text{--->}$$


Ohm:

$$V_{3\Omega} = i_s \times 3 = 6V$$

$$V_{7\Omega} = i_s \times 7 = 14V$$

$$V_{2\Omega} = i_s \times 2 = 4V$$

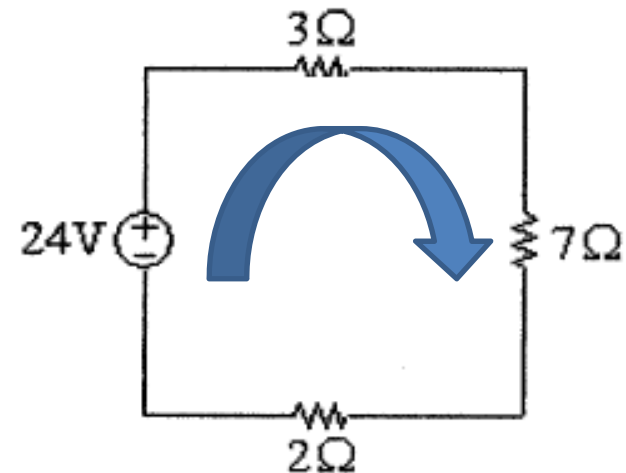
$$P_s = -V_s \times i_s = -24 \times 2 = -48V \text{ (generated)}$$





# Example 5

Find R

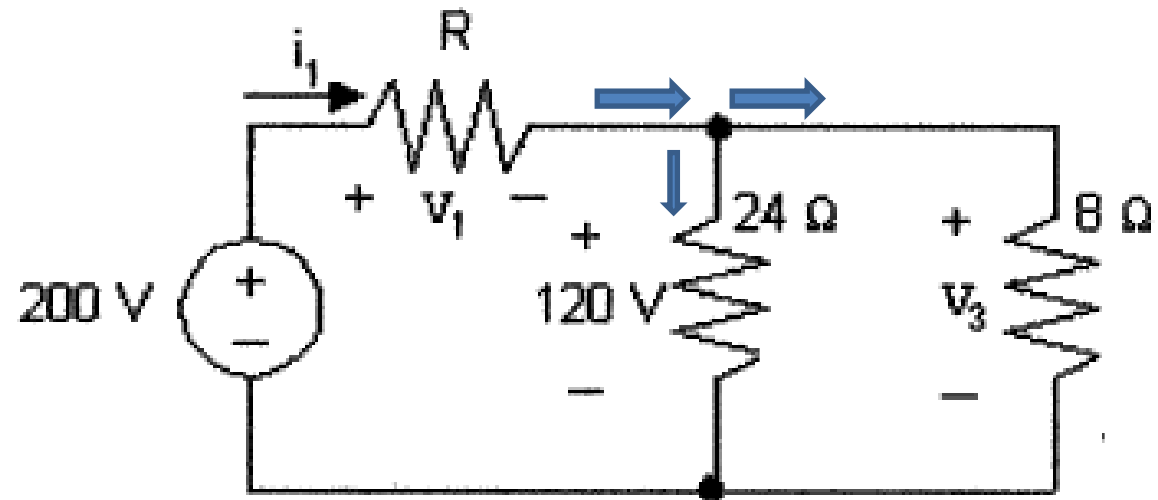

# Example 5 solution

KVL@1:

$$-200 + V_R + 120 = 0$$

$$V_R = 80V$$

KVL@2:

$$-120 + 8i_8 = 0$$

$$i_8 = 120/8 = 15A$$


Ohm:

$$i_{24} = 120/24 = 5A$$

KCL:

$$i_R = i_{24} + i_8$$

$$i_R = 20A$$

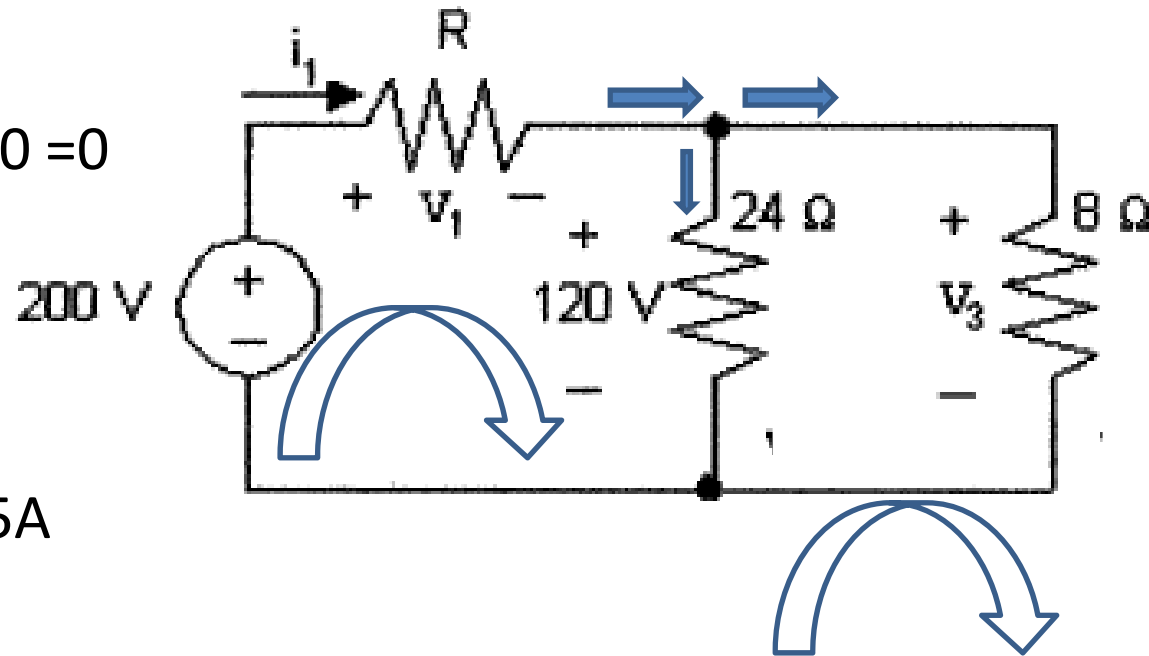

## Example 5 solution (2)

---

Ohm:

$$R = V_R / I_R = 80/20 = 4\Omega$$

---

Thanks,...  
See you next week (ISA),...